

Unit II Applications of Theorems in AC Circuits :-

Thevenin's Theorem :— Any two terminal bilateral linear dc circuit can be replaced by an equivalent circuit consisting of a voltage source and a series resistor.

In AC applications the Thevenin theorem is changed only to include impedance in place of resistance. Since impedances of the circuit are frequency dependent the Thevenin's equivalent circuit found out for a particular network is applicable for only at a specified frequency. Also voltage or current phasors in place of simply real (scalar) voltage or current for independent and dependent sources (with a control variable not in the network under study).

For dependent sources where control variable is governed by the network variable any of the two methods below are used to find the Thevenin's impedance.

Method 1 :— Remove the load impedance. V_{oc} is obtained, next short the load terminals and I_{sc} is determined.

$$\text{Then } Z_{int} = \frac{V_{oc}}{I_{sc}}$$

Method 2 :- Open circuit two load impedances, a source voltage applied across, a source current (I) entering through two load terminals is determined, the original source voltage of the network being set to zero.

The Thevenin's impedance is then given by

$$Z_{int} = \frac{V}{I}$$

$$\text{where } V = V_{oc}$$

Some procedure is followed for finding Norton's equivalent circuit can also be found from each other by using source transformation as explained below:


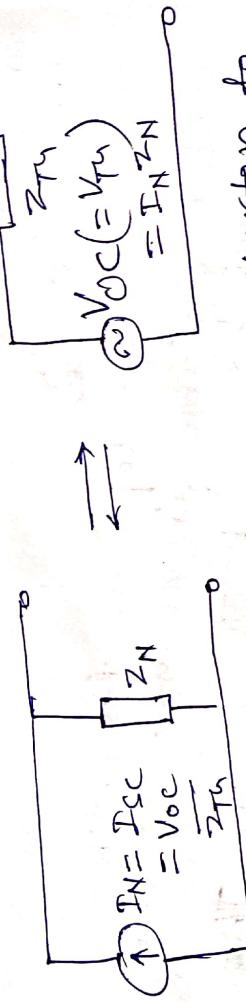


Fig: conversion of Norton to Thevenin and vice-versa.

X 12.19

98 $\Sigma = 33$ $\angle -13^\circ$ A small t_{max} t_{min} t_{max}
W.M. $\angle -13^\circ$ A small t_{max} t_{min} t_{max}

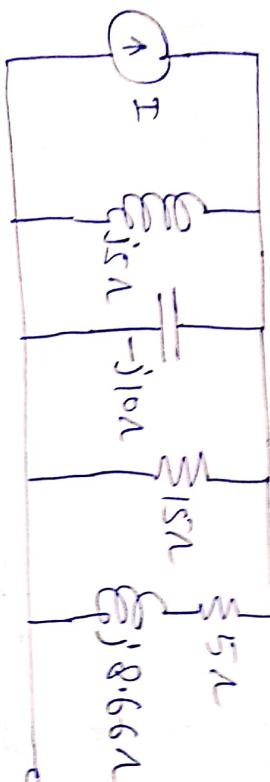~~and~~ ^{old} Valence on the modern
terminally in the modern



Soln:— First find out impedance across current source, let $\text{equivalent admittance}$ be $\frac{Y_{eq}}{V}$, we can write

$$\gamma_{\text{eq}} = \gamma_1 + \gamma_2 + \gamma_3 + \gamma_4$$

$$\text{where } \gamma_1 = \frac{1}{j\zeta} = -j 0.2 \text{ rad/s}$$

$$Y_2 = \frac{1}{-j10} = j0.1 \text{ Wb/A}$$

$$V_3 = \frac{1}{15} = 0.067 \text{ m/s}$$


$$\varphi = \frac{1}{5+18.66} = \frac{1}{10^{16.6^{\circ}}}$$

$$\therefore Y_{eq} = -j^{0.2} + j^{0.1} + 0.067 + 0.05 - j^{0.086} \\ = (0.117 - j^{0.1866}) \text{ mho} = 0.22 \angle -58^\circ$$

$$V_{oc} = \frac{I_{sc}}{R_s + R_{sh}} = \frac{0.22}{0.158} = 1.42$$

To find $Z_{in}(E_{Th})$ open the current source & let $I_{in} = \frac{1}{Y_{eq}} = \frac{1}{0.022} = 45.45 \Omega$

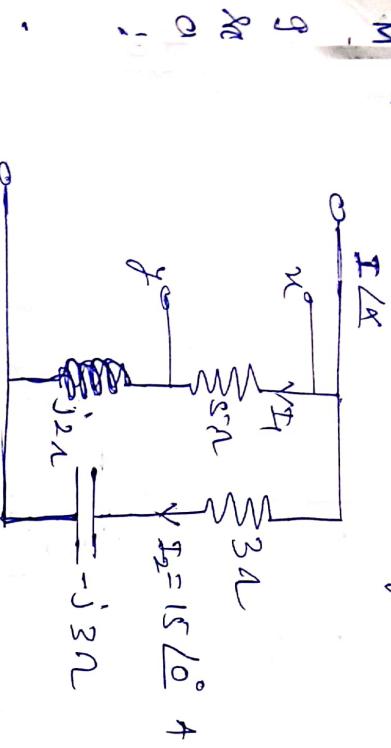Ex 12.2: Using Thevenin's theorem, find the equivalent circuit of the network across $x-y$ in fig below:



Soln:- Given $I_2 = 15 \angle 0^\circ$

drop across $(3-j3)\Omega$

$$\text{V drop} = (3-j3) \times 15 \angle 0^\circ = 63-j6 \angle -45^\circ$$

$$\therefore \text{I}_1 = \frac{\text{V drop}}{5+j2} = \frac{63-j6 \angle -45^\circ}{5+j2} = 11.8 \angle -66.0^\circ$$

$$= (4.64-j10.85) \text{A}$$

$$V_{oc} (= V_{x-y}) = 5 (4.64-j10.85)$$


$$= 59 \angle -66.8^\circ$$

In order to find Z_{in} , open cut the current source, then find Z_{in} looking into terminals $x-y$ as below

$$\therefore Z_{in} = 5\Omega \parallel \frac{(3-j3+j2)}{5+3-j3+j2} = \frac{5(3-j)}{8-j1}$$

$$\begin{aligned} &= \frac{5 * (3-j3+j2)}{15.81 \angle -18.42} = \frac{1.96 \angle 11.29^\circ}{8.06 \angle -71.25^\circ} \\ &= \frac{V_{oc}}{Z_{in}} \end{aligned}$$

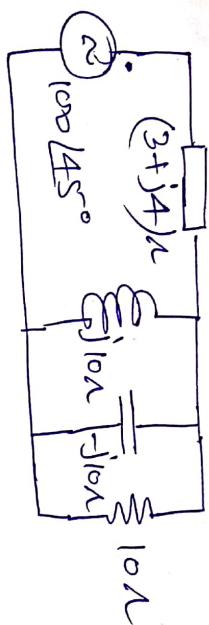12.21. Find the current through 10Ω resistor using Thevenin theorem. Eg below N/A.



Soln :- Remove the load resistance (10Ω), let open circuit voltage be V_{oc} and compute mesh currents as shown below a



$$KVL \text{ in mesh } ①: V_{oc} - j10(i_1 - i_2) = 0$$

$$100 \angle 45^\circ - i_1(3+j4) - j10i_1 + j10i_2 = 100 \angle 45^\circ - -①$$

$$\cancel{100 \angle 45^\circ} \rightarrow (3+j4)i_1 - j10i_2 = 100 \angle 45^\circ$$

$$\text{Similarly in } ②: V_{oc} - j10(i_2 - i_1) = 0$$

$$-(-j10)i_2 - i_1(3+j4) - j10i_2 + j10i_1 = 0$$

$$j10i_2 - j10i_2 + j10i_1 = 0$$

$$\Rightarrow i_1 = 0 - -②$$

$$\text{put in eqn } ① \\ -j10i_2 = 100 \angle 45^\circ$$

$$\text{or } i_2 = -\frac{10}{j} \angle 45^\circ = 10 \angle 135^\circ$$

$$10 \angle 135^\circ \text{ A}$$


check?

$$V_{a-b} (= V_{oc}) = -j10 \times 10 \angle 45^\circ = j100 \angle 45^\circ$$

Internal impedance

$$Y_{int} = \frac{1}{-j10} + \frac{1}{j10} + \frac{1}{3+j4}$$

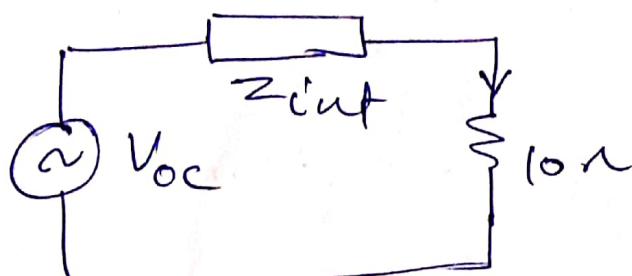
$$\therefore Z_{int} = \frac{1}{Y_{int}} = (3+j4) \Omega$$




\$\therefore\$ current in \$10\Omega\$ resistor

$$= \frac{V_{oc}}{Z_{int} + 10} = \frac{100 \angle 45^\circ}{3+j4+10} = 7.35 \angle 28.3^\circ A$$

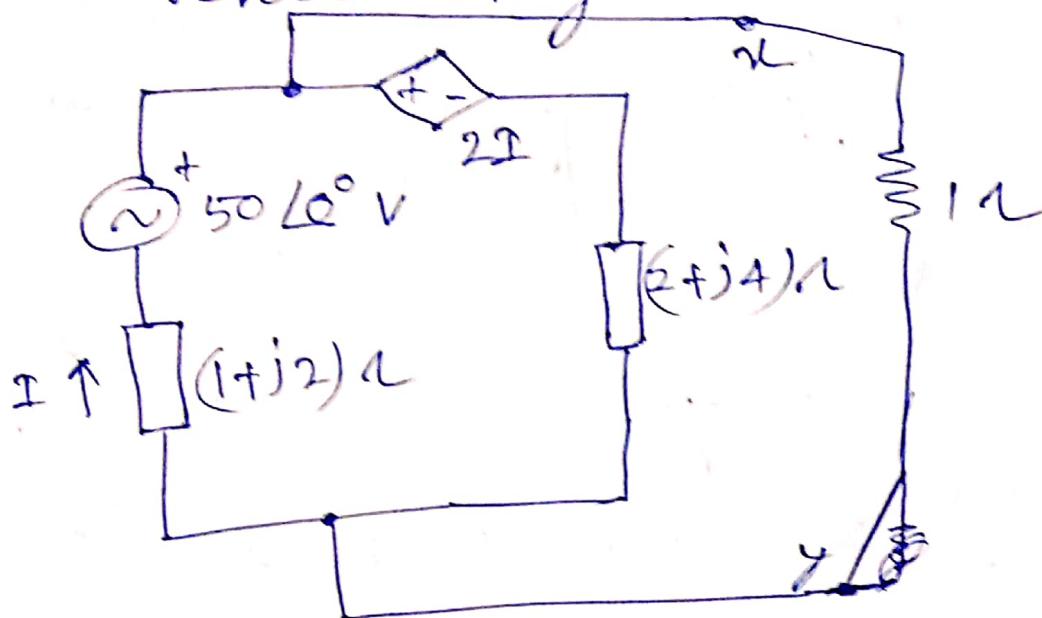X12.31 :- Find Thevenin's equivalent network of the circuit below across $x-y$ and find the current through the 1Ω resistor. Verify the result using Norton's theorem.



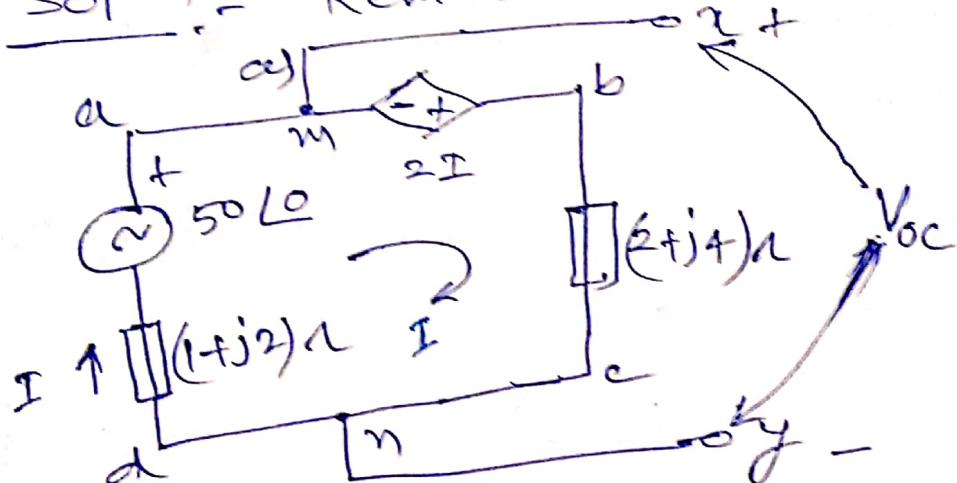Solⁿ :- Remove 1Ω resistor, the circuit becomes



Applying KVL in loop abcd'a

$$50 + 2I - I(1+j2 + 2+j4) = 0$$

$$50 + 2I - I(3+j6) = 0 \Rightarrow 50 - I(1+j6) = 0$$


$$\Rightarrow I = \frac{50}{1+j6} = (1.35 - j8.11) A$$

from observation of circuit

$$V_{oc} = V_{xy} = V_{mn} = -I(1+j2) + 50$$

$$= -(1.35 - j8.11)(1+j2) + 50$$
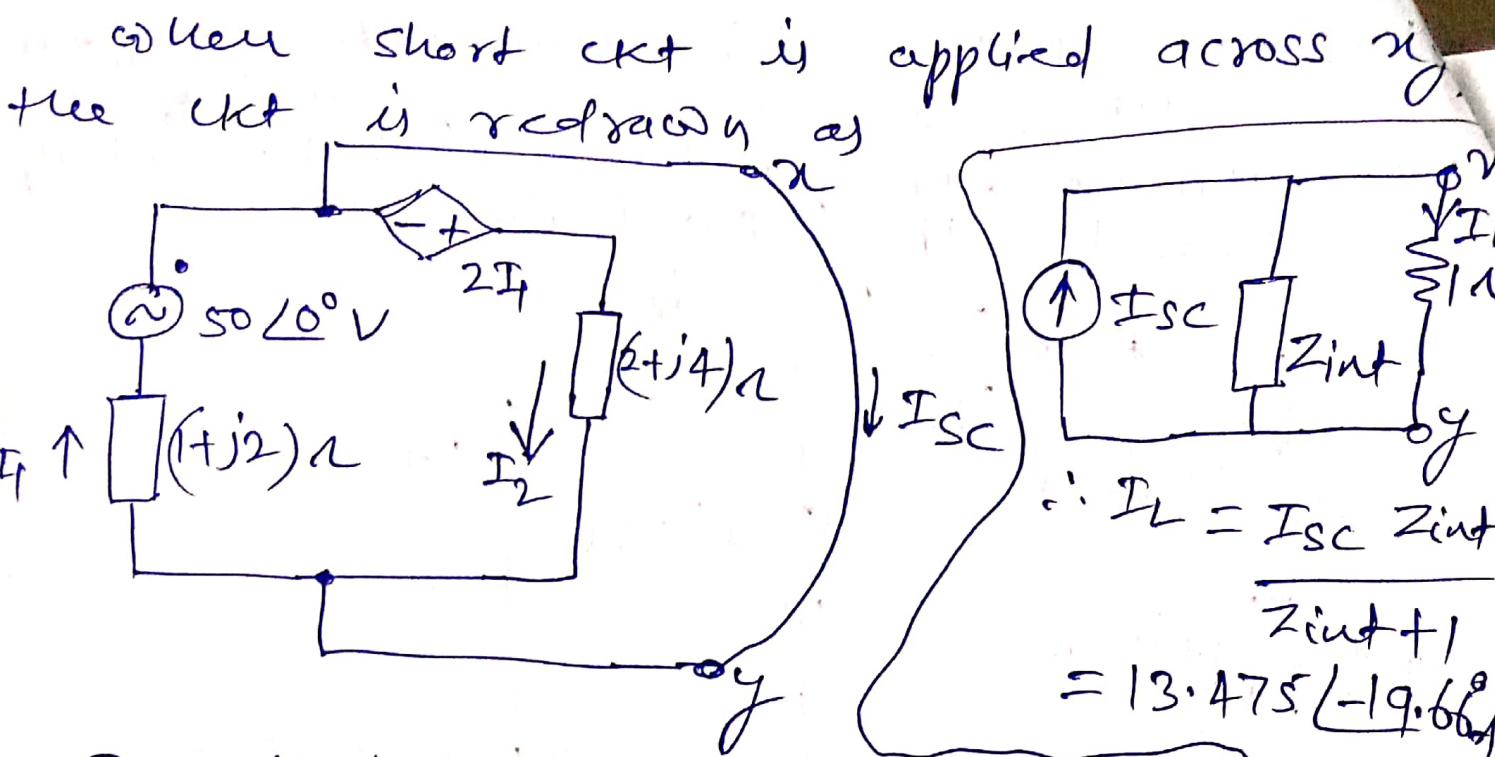
$$V_{oc} = (32.43 + j54.11)V = 32.48 \angle 45.5^\circ$$



$$I_1 = \frac{50 \angle 0^\circ V}{(+j2)\Omega} = 22.36 \angle -63.43^\circ A \quad \text{verified}$$

and $I_2 = \frac{2I_1 V}{(2+j4)\Omega} = \frac{2 \times 22.36 \angle 63.43^\circ}{4.472 \angle 63.43^\circ} = 10 \angle -126.87^\circ A$


$$\therefore I_{SC} = I_1 - I_2 = 22.36 \angle -63.43 - 10 \angle -126.87^\circ = 20 \angle -36.87^\circ A$$

$$\therefore Z_{int} = \frac{V_{OC}}{I_{SC}} = \frac{32.88 \angle -9.47^\circ}{20 \angle -36.87^\circ} = 1.644 \angle 46.34^\circ$$


\therefore previous's eqnt is

$\therefore I_L$ current through \$Z_{int}
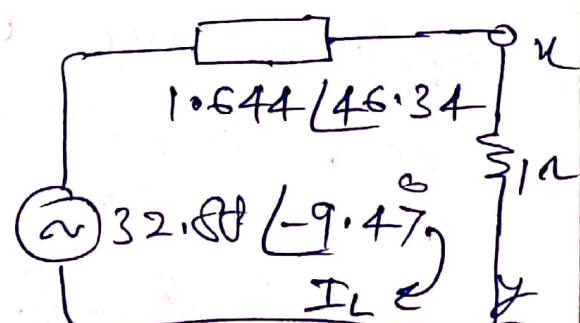
$$\text{resistor} = \frac{32.88 \angle -9.47^\circ}{1.644 \angle 46.34^\circ + 1} = 13.475 \angle -19.66^\circ A$$



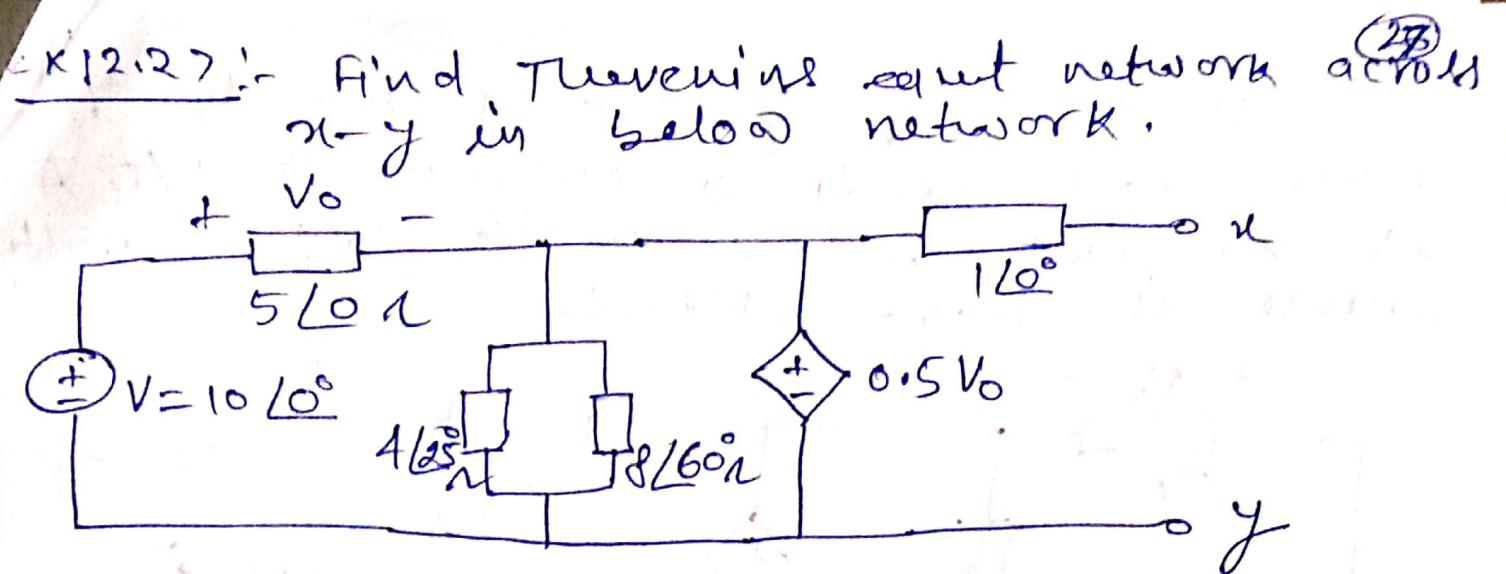
To validate it by Norton's theorem, Norton's eqnt is redrawn as \$I_{SC}\$ & \$Z_{int}\$ already calculated.



Soln:- Parallel combination of $4\angle 25^\circ \Omega$ & $8\angle 60^\circ \Omega$, $Z = \frac{4\angle 25^\circ \times 8\angle 60^\circ}{4\angle 25^\circ + 8\angle 60^\circ}$

$$Z = 2.78\angle 36.5^\circ \Omega$$

Simplified ckt is as below

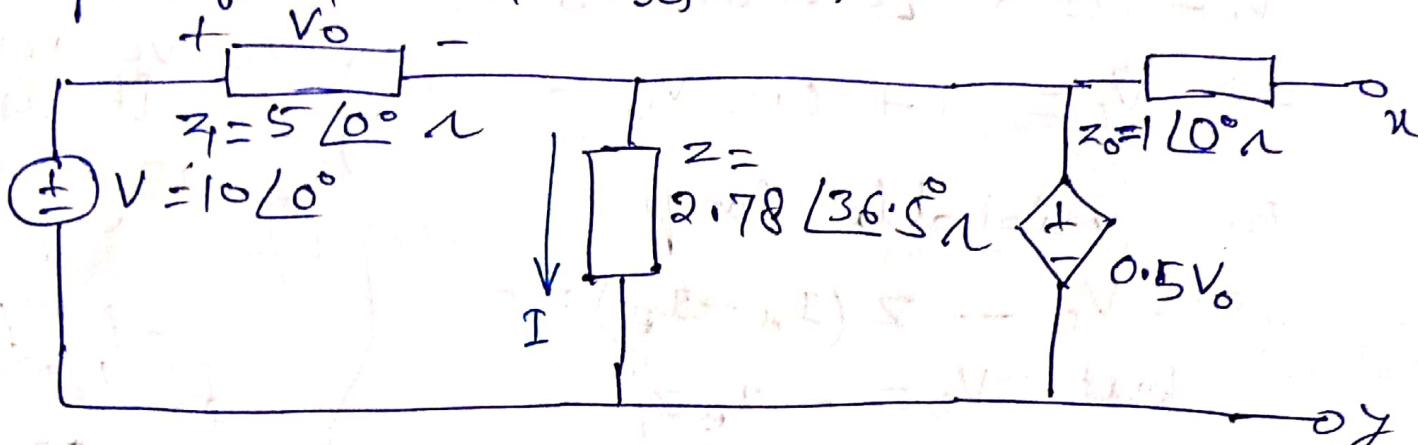

Let the current through Z be I , we observe that $Iz = 0.5V_0 = -V_{oc}$

Also in leftmost loop


$$10\angle 0^\circ - V_o - 0.5V_0 = 0 \Rightarrow 10 - 1.5V_0 = 0$$

$$\Rightarrow V_o = \frac{10}{1.5} = 6.67V_0 \text{ (dp)}$$

$$\therefore V_{oc} = 0.5V_o = 0.5 \times 6.67\angle 0^\circ = 3.335\angle 0^\circ$$

$$V_{oc} = 3.335\angle 0^\circ \text{ Volts}$$

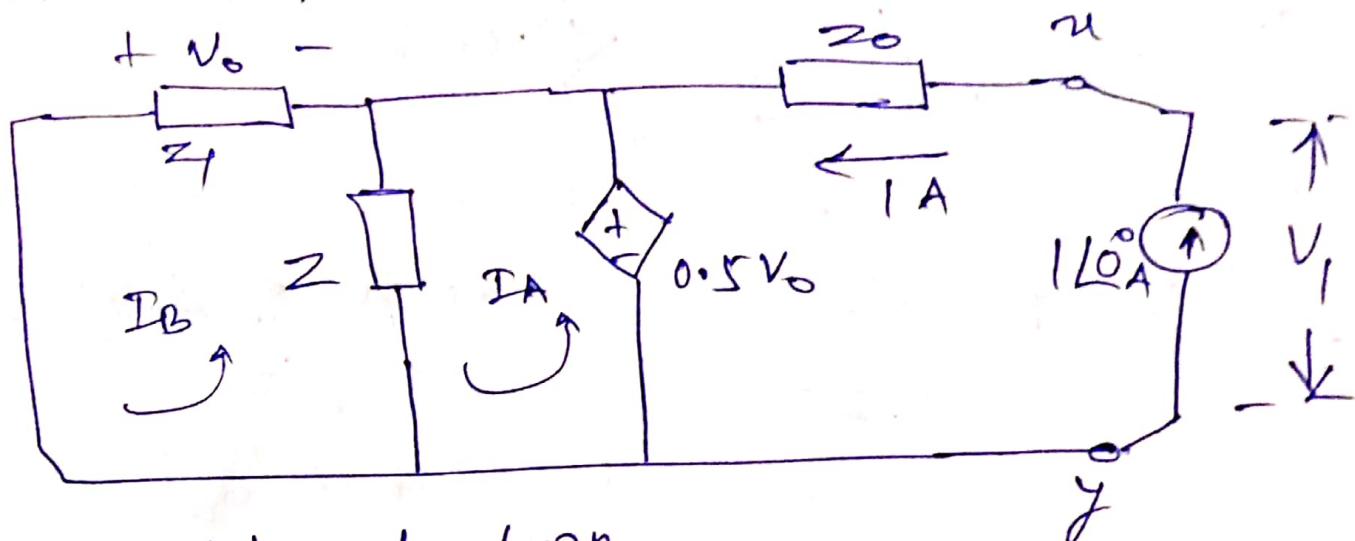To find Z_{int} let a voltage V_1 apply across $x-y$ sends a current of $120^\circ A$ as in circuit below while original voltage source is short circuited.



in rightmost loop

$$V_1 - 120 \times 120 - 0.5 V_0 = 0$$

$$\Rightarrow V_1 = 1 + 0.5 V_0 \quad \text{--- (1)}$$

in middle loop

$$0.5 V_0 - Z (I_A - I_B) = 0$$

$$\text{but } V_0 = - I_B Z_1$$

$$\therefore -0.5 (I_B Z_1) - Z (I_A - I_B) = 0$$

$$\text{or } 0.5 I_B Z_1 + Z (I_A - I_B) = 0$$

$$\text{or } I_B (0.5 Z_1 - Z) + I_A Z = 0 \quad \text{--- (2)}$$

Again in leftmost loop


$$+V_0 Z - (I_B - I_A) Z + I_B Z_1 = 0$$

$$\text{or } (I_B - I_A) Z + I_B Z_1 = 0 \quad \text{or } I_B (Z_1 + Z) - I_A Z = 0 \quad \text{--- (3)}$$

from (2) put value of $I_A Z$ in (3) & simplify we get $I_B = 0$ $\therefore V_0 = - I_B Z_1 = 0$. put in (1)

$$V_1 = 1 V. \therefore Z_{int} = \frac{V_1 (V_0 +)}{120^\circ A} = 1 \Omega$$

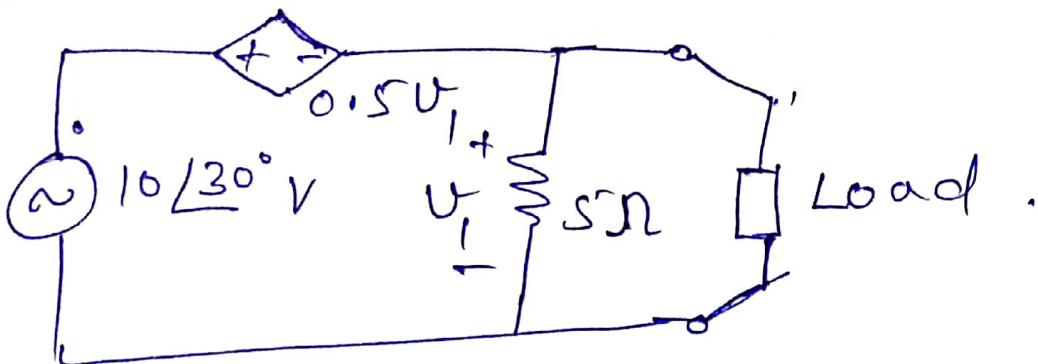Ex 12.29 :- Find Thevenin's eqnt ckt of the network shown below:



Soln:- Remove the load, the $V_{OC} = U_1$
Apply KVL in left loop



$$10 \angle 30^\circ - 0.5U_1 - U_1 = 0$$

$$10 \angle 30^\circ - 1.5U_1 = 0 \Rightarrow U_1 = \frac{10 \angle 30^\circ}{1.5}$$

~~$$U_1 = 6.67 \angle 30^\circ V$$~~


$$\therefore V_{OC} = 6.67 \angle 30^\circ V$$

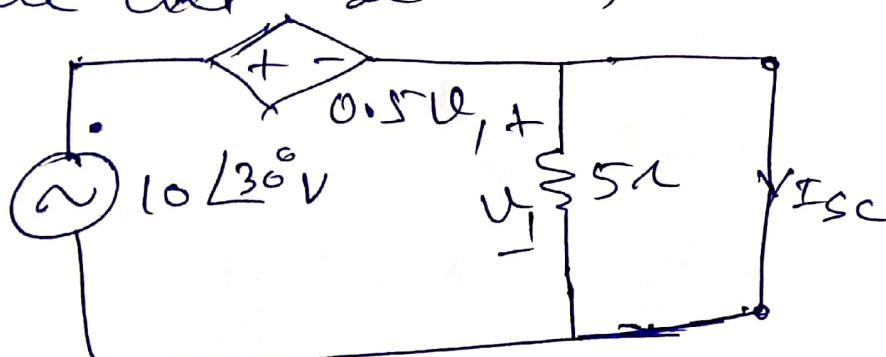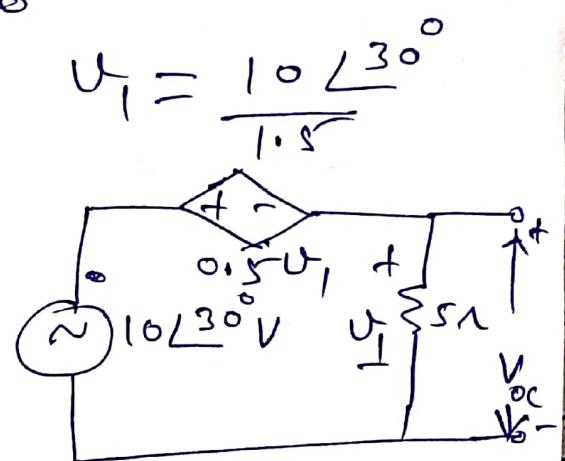Now short circuiting the load terminals, the ckt becomes



When load is shorted whole current will flow through short circuit & $U_1 = 0$ hence

KVL gives

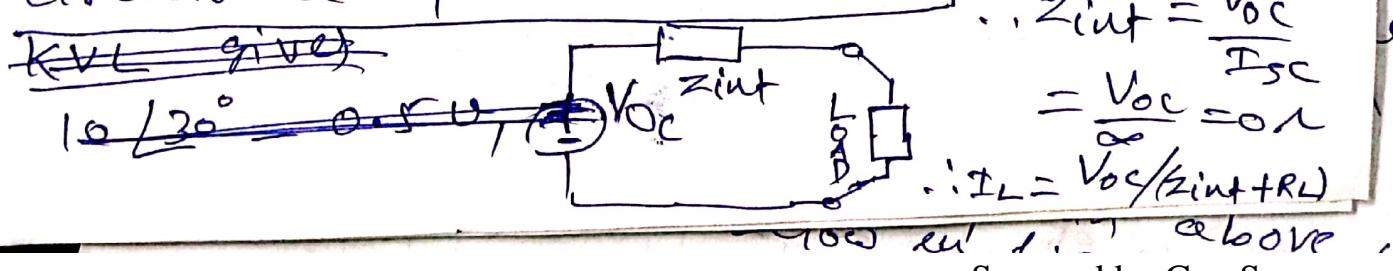

hence

$$I_{SC} = \frac{10 \angle 30^\circ - 0}{0}$$

∴ no impedance in ckt

$$\therefore I_{SC} = \infty$$


$$\therefore Z_{int} = \frac{V_{OC}}{I_{SC}}$$

$$= \frac{V_{OC}}{\infty} = 0 \Omega$$


$$\therefore I_L = \frac{V_{OC}}{Z_{int} + R_L}$$

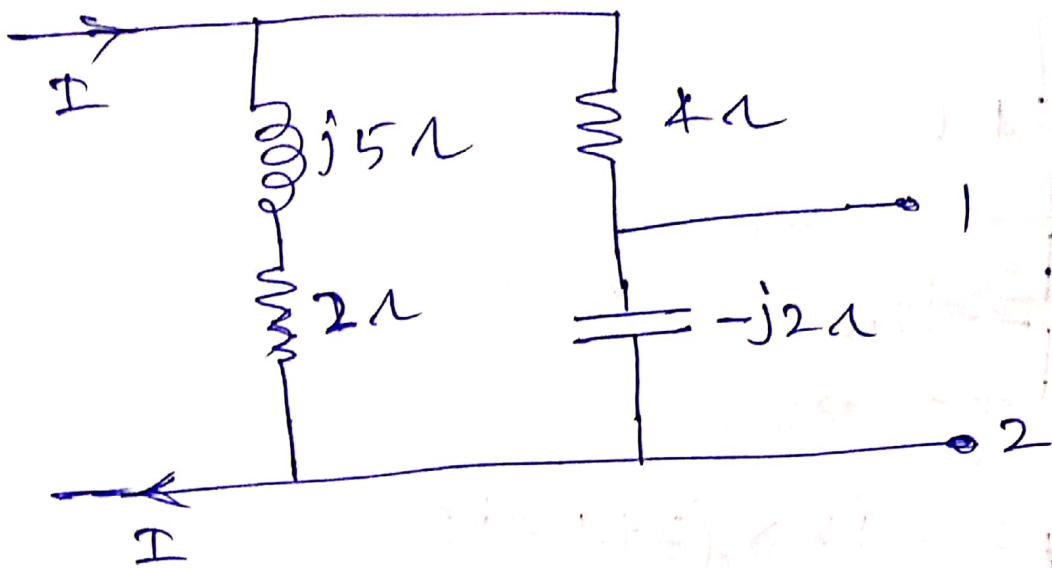(29)

Ex 12.26! - Find Norton's equivalent for the network shown below at the left of terminals 1-2, assume $I = 5 \angle 0^\circ A$.



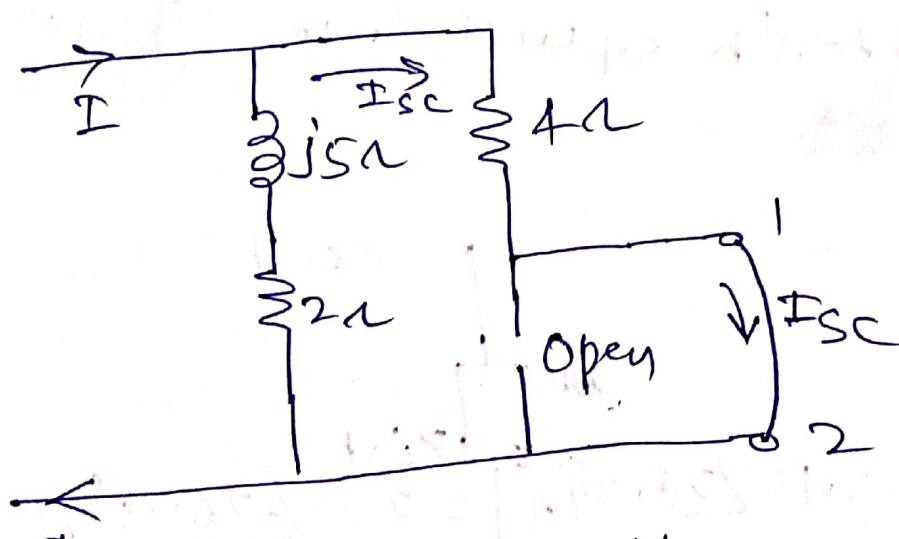Sol'n! - as the terminals 1-2 are shorted no current flows through $-j2\Omega$ reactance & act it as below




from observation

$$I_{sc} = \frac{I(2+j5)}{2+j5+4} = \frac{5 \angle 0^\circ (2+j5)}{6+j5}$$

$$= 3.45 \angle 28.39^\circ A$$

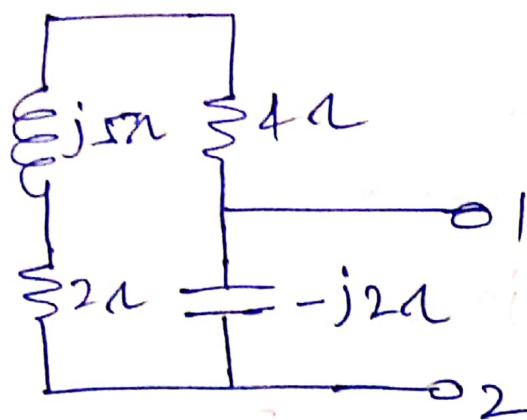
To determine the internal impedance, open circuit the current source & see from terminals 1-2 to left.



$$\therefore Z_{int} = \frac{-j2 \times (2+4+j5)}{-j2 + 2+4+j5}$$

$$= 2.33 \angle -76.75^\circ \Omega$$

∴ Norton's equivalent is as below:

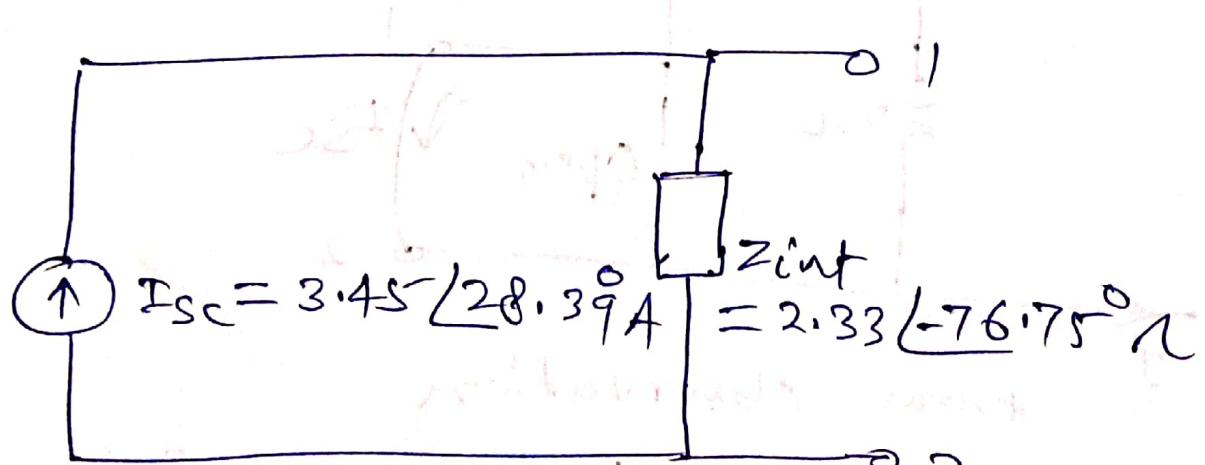

Superposition Theorem for AC Networks

For DC networks

If a no. of voltage or current sources are active simultaneously in a linear network, the resultant current in any branch is the algebraic sum of currents that would be produced in it, when each source ^{independently} acting alone replacing all other ^{independent} sources by their internal impedances.

for AC Networks :- For superposition theorem with AC networks even with AC networks with independent sources, circuit will have to be worked out with impedances & phasors (operation with complex nos) instead of just resistors & real nos. in same way as for DC networks.

For dependent sources in which the control variable is determined by the net work to which the theorem is to be applied, the dependent source can't get to fixed, the dependent source controlling variable is be zero unless controlling variable is also zero.

For networks where both the independent and dependent sources exist, the superposition theorem is to be applied for each independent source and for each dependent source not having a controlling variable in the portion of net work under consideration.

In order to explain above, consider the circuit below in fig ①

In fig (a), both the sources have control variable V & I but it is to be noted that V & I does not make the source dependent on the variable of any portion of the network and each source can be treated as independent source.

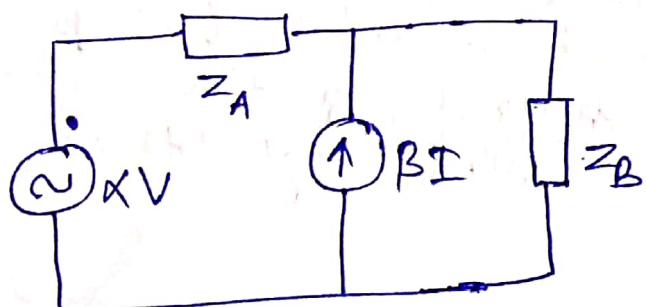


fig (a)

To apply superposition theorem

To calculate current through ZB let remove current

xV , then consider voltage source source BI & current through ZB


$$I' = \frac{xV}{Z_A + Z_B}$$

Now consider current source BI & ~~short voltage source xV~~ , the current through ZB is


$$I'' = BI \frac{Z_A}{Z_A + Z_B}$$

∴ Net current, by superposition = $I' + I''$

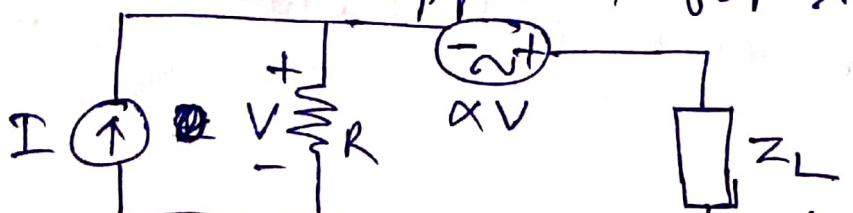
Now consider the fig (b) below, it may be noted that the controlling variable V is determined by the network to be analyzed. If the current source is set to zero the drop across R would vanish and this will make $xV = 0$, thus the user would then lack of any source thus superposition theorem can not be applied for such sources.



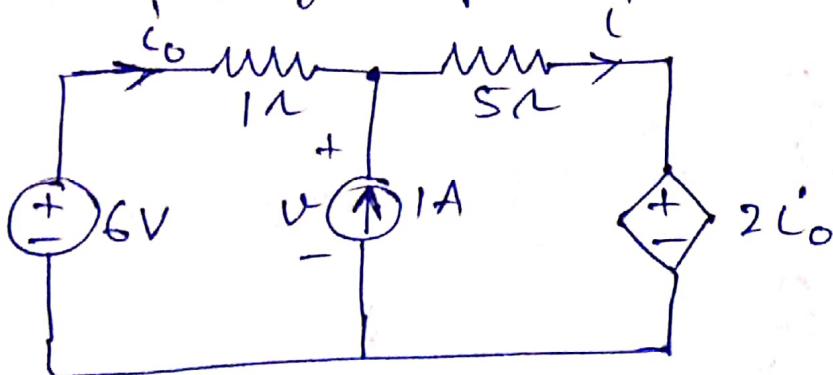Q3.45 :- Find i'_0 and i' from the circuit below using superposition theorem. (3)




Soln:- Assuming 6V source to be active

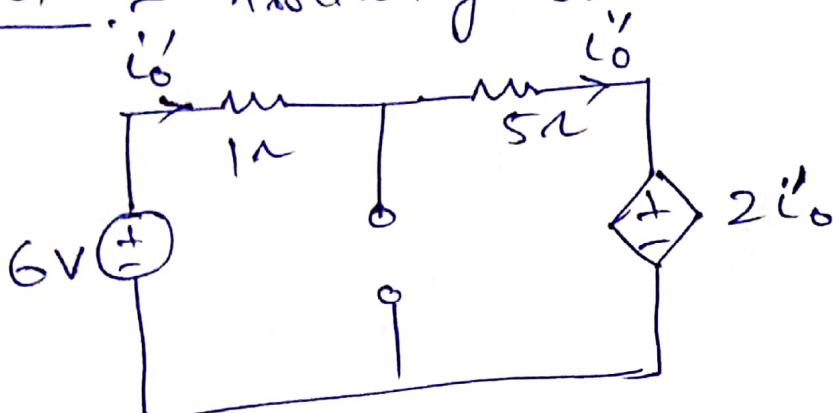

$$\begin{aligned} \text{KVL gives} \\ 6 - 6i''_0 - 2i''_0 = 0 \\ \Rightarrow 8i''_0 = 6 \\ i''_0 = \frac{6}{8} = \frac{3}{4} \text{ A} \end{aligned}$$

Now considering 1A source active

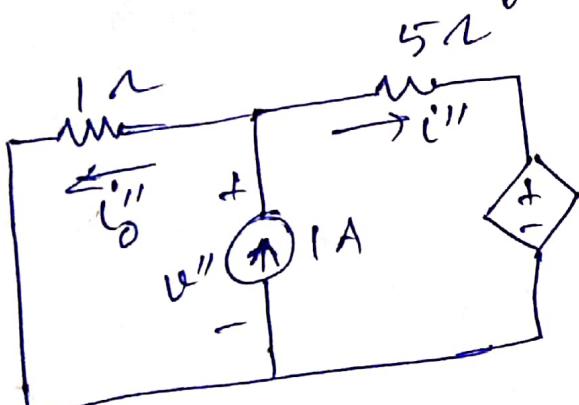

$$\begin{aligned} \text{KCL gives} \\ i = i''_0 + i'''_0 \\ = \frac{v''}{1} + \frac{v'' - 2i''_0}{5} \\ = v'' + 0.2v'' - 0.4i''_0 \\ = 1.2v'' - 0.4i''_0 \end{aligned}$$

$$\text{but } i''_0 = \frac{v''}{1} \Rightarrow \cancel{v''} = i''_0$$

$$\therefore i = 1.2i''_0 - 0.4i''_0 = 0.8i''_0$$


$$\begin{aligned} \Rightarrow i''_0 &= \frac{1}{0.8} = 1.25 \text{ A} & \& i''_0 = \frac{v'' - 2i''_0}{5} \\ \therefore i'''_0 &= -\frac{1.25}{5} = -0.25 \text{ A} & = \frac{i''_0 - 2i''_0}{5} = -\frac{i''_0}{5} \end{aligned}$$

Hence using superposition theorem


$$i_0 = i'_0 - i''_0 = \frac{3}{4} - 1.25 = 0.75 - 1.25 \\ = -0.50 \text{ A}$$
$$\& i = i''_0 + i'' = \frac{3}{4} - 0.25 = 0.75 - 0.25 \\ = 0.50 \text{ A}$$

(34)

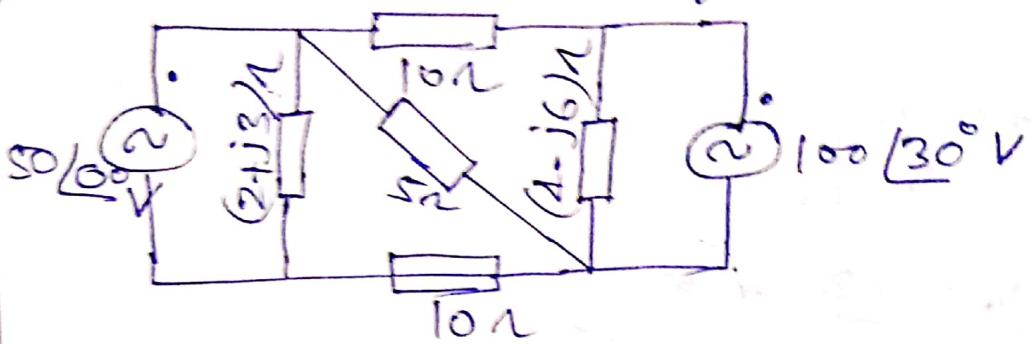Q12.38 :- Find by superposition theorem, the current through 5Ω resistor in fig below.



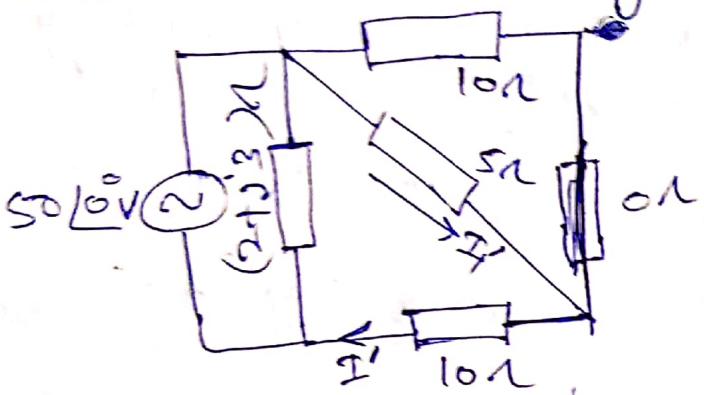Sol^u :- Deactivating $100 \angle 30^\circ V$ source, the ckt is



since short circuit across $(4-j6)\Omega$ makes it zero.

$$I' = \frac{50 \angle 0^\circ}{(10 \parallel 5) + 10} = 3.75 \angle 0^\circ A$$


$\therefore (10 \parallel 5) + 10$ is in parallel with $(2+j3)\Omega$.
 \therefore same voltage appears across $(10 \parallel 5) + 10 \Omega$.

$$\text{and } I'_1 = \frac{I'}{10+5}$$

$$= 3.75 \angle 0^\circ \times \frac{10}{15}$$

$$= 2.5 \angle 0^\circ A$$

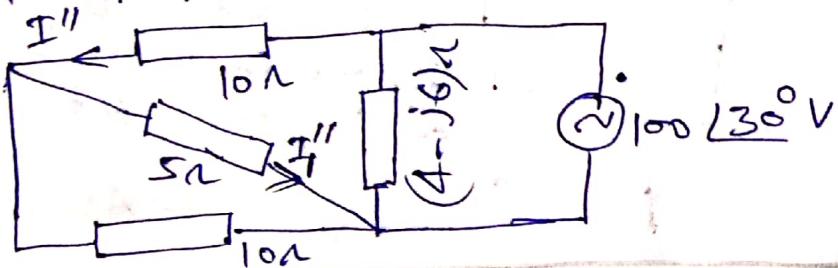Again deactivate $50 \angle 0^\circ V$ source and consider the other source, ckt is as below:



$$= \sqrt{R_{eq}} \angle 30^\circ$$


$$\therefore I'' = \frac{100 \angle 30^\circ}{10 + 15 + j0} = 7.5 \angle 30^\circ A$$

$$\begin{aligned}\therefore I'' &= I'' \frac{10}{5+10} \\ &= 7.5 \angle 30^\circ A \times \frac{10}{15} \\ &= 5 \angle 30^\circ A\end{aligned}$$


\therefore current through 5Ω resistor, using principle of superposition is

$$\begin{aligned}I_{(5\Omega)} &= I'_1 + I'' = 2.5 \angle 0^\circ + 5 \angle 30^\circ \\ &= 6.83 + j2.5 = 7.273 \angle 20.1^\circ A\end{aligned}$$

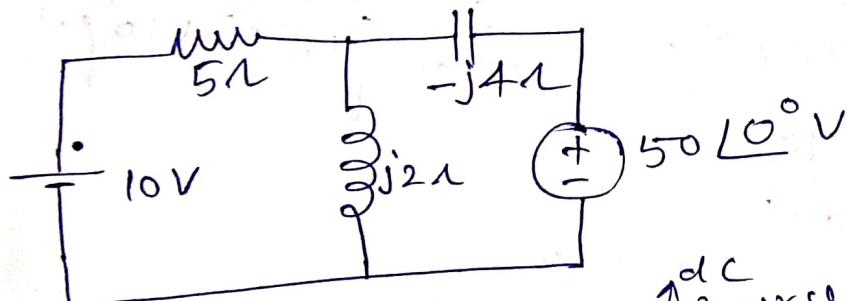Ex 12.36:- obtain the steady state current through the $10V$ battery in time domain in the circuit of fig below using superposition theorem.



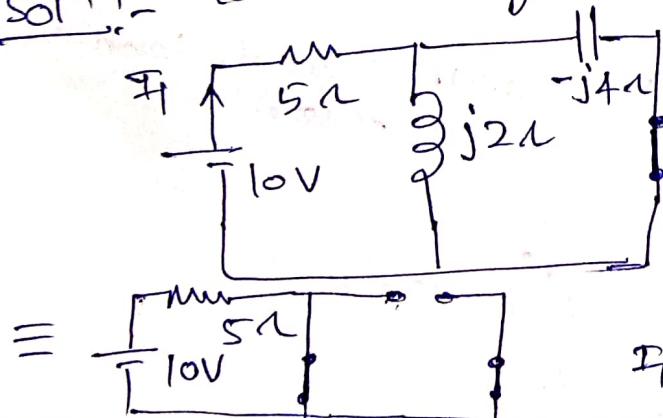Sol'n:- considering $10V$ \uparrow^{dc} source initially




with dc source
 $j2\Omega$ inductive reactance behave as short circuit and $-j4\Omega$ capacitive behave as open circuit hence

$$I = \frac{10}{5} = 2 A$$

$$= \frac{0}{(R_g + R_L) + j(Y_g + Y_L)}$$

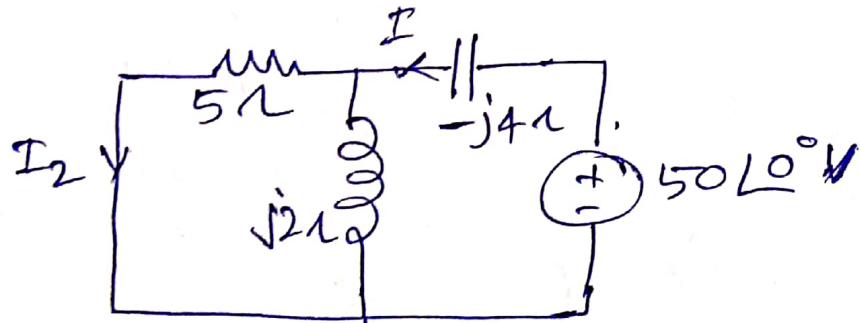Now consider $50 \angle 0^\circ$ V ac source only
then



$$Z = -j4\Omega + \frac{5 \times j2}{5 + j2} = \left(\frac{8-j10}{5+j2} \right) \Omega$$

$$= 12.8 \angle -51.34^\circ$$

$$= \frac{5.385 \angle 21.8^\circ}{2.377 \angle -73.14^\circ}$$

$$\therefore I = \frac{50 \angle 0^\circ}{2.377 \angle -73.14^\circ} = 21.04 \angle 73.14^\circ$$

$$\therefore I_2 = \frac{I \angle 21.8^\circ}{5 + j2} = \frac{21.04 \angle 73.14^\circ \angle 21.8^\circ}{5 + j2}$$

$$= 7.81 \angle 141.34^\circ$$

in time domain instantaneous value is

$$i_2 = I_m \sin(\omega t + \theta)$$

$$= 7.81 \times \sqrt{2} \sin(\omega t + 141.34^\circ)$$

$$= 11 \sin(\omega t + 141.34^\circ)$$

\therefore Net current through the + current is

10V battery in time domain is


$$= 2 - 11 \sin(\omega t + 141.34^\circ)$$

Ans


since 2 A current is due to battery
i.e. dc current i.e. average value
no instantaneous value.

Here $I' = \frac{V_o}{R_{Th} + (R_L + \Delta R_L)}$

(3)

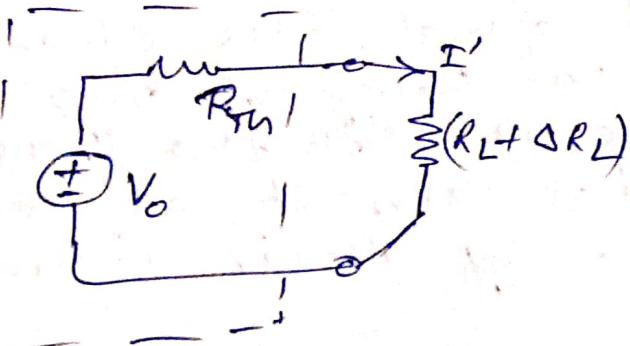

Thevenin's
equivalent source

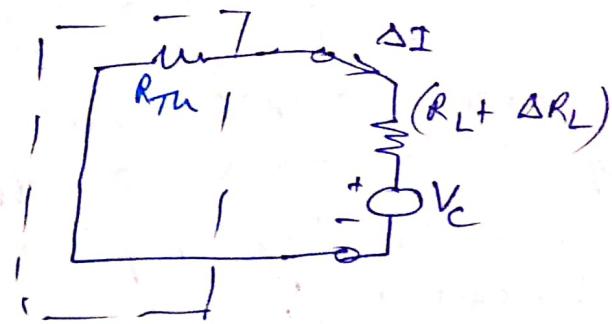

Source Network
with source replaced
by internal resistance

fig ⑥ : Explanation of Compensation
Theorem.

The change of current being denoted by ΔI , we get

$$\begin{aligned}\Delta I &= I' - I \\ &= \frac{V_o}{R_{Th} + (R_L + \Delta R_L)} - \frac{V_o}{R_{Th} + R_L} \\ &= V_o \left\{ \frac{R_{Th} + R_L - (R_{Th} + R_L + \Delta R_L)}{(R_{Th} + R_L + \Delta R_L)(R_{Th} + R_L)} \right\} \\ &= - \left(\frac{V_o}{R_{Th} + R_L} \right) \frac{\Delta R_L}{(R_{Th} + R_L + \Delta R_L)} \\ &= - \frac{I \Delta R_L}{R_{Th} + R_L + \Delta R_L} = - \frac{V_c}{R_{Th} + R_L + \Delta R_L}\end{aligned}$$

where $V_c = I \Delta R_L$ is termed as compensating voltage.

~~... Then ...~~

Thus it has been proved that with the change of branch resistance, branch current is changed and the change is equal to an ideal compensating voltage source in series with the branch opposing the original current, all other sources being replaced by their external resistances.

(34)

Tellegen's Theorem:- In any linear, non-linear, passive, active time variant network, excited by ac sources, the summation of instantaneous or complex power of the sources is zero.

For a network excited by sinusoidal sources, if no. of branches be 'b',

$$\sum_{b=1}^B V_b i_b = 0$$

where V_b and i_b represent the instantaneous voltage and current of source at each branch

When considering complex power, if V_b and I_b be the voltage and current of each branch then as per this theorem

$$\sum_{b=1}^B V_b I_b^* = 0$$

Where I_b^* \rightarrow complex conjugate of I_b

Proof of Tellegen's theorem:- For the network shown below let the node voltages be V_1 , V_2 and V_3 at nodes 1, 2 & 3 respectively. The current directions are shown arbitrarily.

Fig. 4

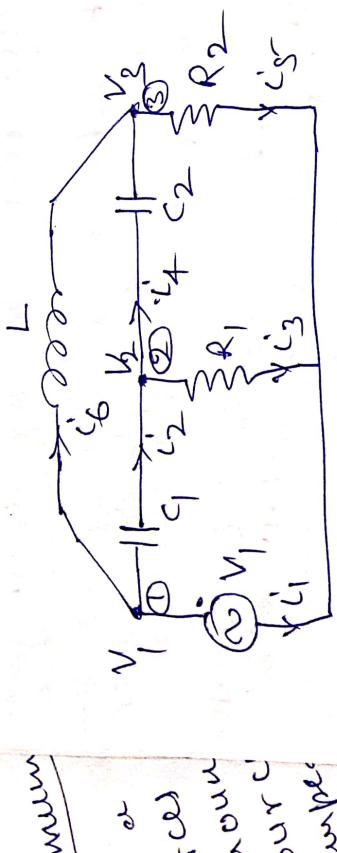


Fig: Application of Tellegen's theorem
The summation of instantaneous power
in the network is given by
Proof

$$\begin{aligned} \sum_{b=1}^6 V_b i_b &= V_1 i_1 + V_{c_1} i_2 + V_{R_1} i_3 + V_{C_2} i_4 + V_{R_2} i_5 \\ \text{or } \sum_{b=1}^6 V_b i_b &= V_1 i_1 + (V_1 - V_2) i_2 + V_2 i_3 + (V_2 - V_3) i_4 \\ &\quad + V_3 i_5 + (V_1 - V_3) i_6 \\ &= V_1 (i_1 + i_2 + i_6) + V_2 (i_3 - i_2 + i_4) + V_3 (i_5 - i_4) \end{aligned}$$

Applying KCL at node ① gives
and at node ②

$$i_3 + i_4 - i_2 = 0$$


$$i_5 - i_4 - i_6 = 0$$

thus finally,

$$\sum_{b=1}^6 V_b i_b = V_1 x_6 + V_2 x_0 + V_3 x_0 \\ = 0$$

\therefore The Tellegen's theorem is proved.

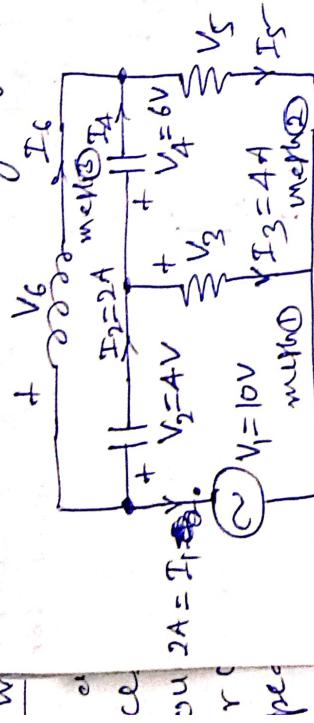12.4.6: In the network shown below, check the validity of Tellegen's theorem.



Soln: - Let us first find unknown voltage and currents. KVL in mesh ①

$$10 - 4 - V_3 = 0 \Rightarrow V_3 = 10 - 4 = 6V$$

KVL in mesh ②

$$6 - 6 - V_5 = 0 \Rightarrow V_5 = 0V$$

KVL in mesh ③

$$4 - V_6 + 6 = 0 \Rightarrow V_6 = 10V$$

Next apply KCL at node ①

$$2 + 2 + I_6 = 0 \Rightarrow I_6 = -4A$$

KCL at node ②

$$4 + I_4 - 2 = 0 \Rightarrow I_4 = -2A$$

KCL at node ③

$$I_5 - I_4 - I_6 = 0 \Rightarrow I_5 + 2 + 4 = 0 \Rightarrow I_5 = -6A$$

$$\text{Now } \sum_{k=1}^6 V_k i_k = V_1 I_1 + V_2 I_2 + V_3 I_3 + V_4 I_4 + V_5 I_5 + V_6 I_6 \\ = 10 \times 2 + 4 \times 2 + 6 \times 4 + 6 \times (-2) + 0 \times (-6) + 10 \times 4 \\ = 20 + 8 + 24 - 12 + 0 - 40 \\ = 52 - 52 = 0 \therefore \text{Proved}$$

57

Transistor energy theorem:-

Ex:- use compensation theorem to solve
when change in current through
load resistance is known then
change in current by ΔI is
incarved by ΔR_L below:



Soln:- As per compensation theorem
the change in current

$$\Delta I = \frac{V_c}{R_{Th} + R_L + \Delta R_L} = \frac{\Delta R_L}{R_{Th} + R_L + \Delta R_L}$$

Nowhere $V_c = I \cdot \Delta R_L$

$$I = \frac{V_c}{Z_{int} + R_L} = \frac{100}{4 + 10} = \frac{100}{14} = 7.14 \text{ A}$$

$$\therefore \text{Change in current} \\ = \frac{7.14 \times 1}{4 + 10 + 1} = \frac{7.14}{15} = \underline{\underline{0.4764}}$$

Maximum Power Transfer Theorem:

In a linear network having energy sources and impedances, the maximum amount of power is transferred from source to load impedance if the load impedance is the complex conjugate of the total impedance of the network.

Proof :- Consider ckt below having load impedance Z_L and source impedance Z_g , connected in series with the source V_g . Let I be the current through load.

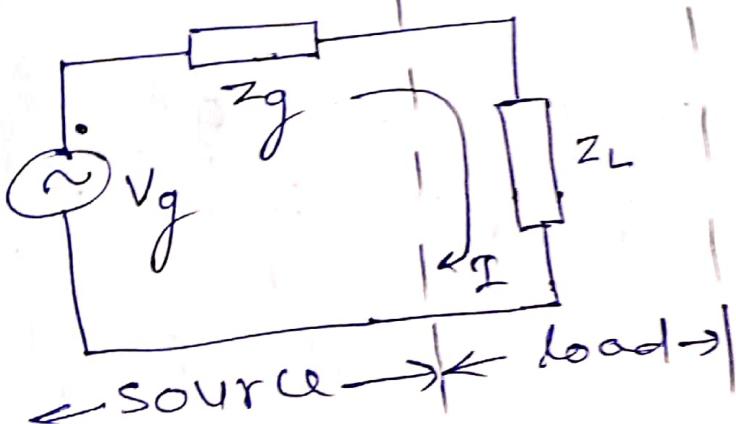


Fig: ckt for Maximum Power Transfer Theorem.

From above ckt

$$\begin{aligned} I &= \frac{V_g}{Z_g + Z_L} = \frac{V_g}{(R_g + jX_g) + (R_L + jX_L)} \\ &= \frac{V_g}{(R_g + R_L) + j(X_g + X_L)} \end{aligned}$$

In Real Power, $P_L = I^2 R_L$

$$P_L = \frac{V_g^2}{(R_g + R_L)^2 + (X_g + X_L)^2} \cdot R_L \quad \text{--- (1)}$$

for maximum power flow from source to load

$$\frac{d P_L}{d X_L} = 0$$

$$\Rightarrow \frac{d P_L}{d X_L} = \frac{d}{d X_L} \left(\frac{V_g^2 R_L}{(R_g + R_L)^2 + (X_g + X_L)^2} \right)$$

$$\frac{d P_L}{d X_L} = - \frac{V_g^2 R_L \cdot 2(X_g + X_L)}{\left[(R_g + R_L)^2 + (X_g + X_L)^2 \right]^2} \quad \text{--- (2)}$$

Put $\frac{d P_L}{d X_L} = 0$ and simplifying

we get $X_g = -X_L$

Now put $X_g = -X_L$ in eqn (1)

$$P_L = \frac{V_g^2 R_L}{(R_g + R_L)^2} = \frac{V_g^2}{4 R_g} \left[1 - \left(\frac{R_g - R_L}{R_g + R_L} \right)^2 \right]$$

$$P_L = \frac{V_g^2}{4 R_g} \left[1 - \left(\frac{R_g - R_L}{R_g + R_L} \right)^2 \right]$$

(A)

It may be proved that P_L attains maximum value when $R_L = R_g$. Thus maximum power transfer is possible only when

$$R_g + jX_g = R_L - jX_L$$

i.e.

$$Z_g = Z_L^*$$

Z_L^* → complex conjugate of Z_L

and amount of maximum power transfer becomes


$$P_{L,\max} = \frac{V_g^2}{4R_L}$$

4. Find of the

In solving, the problem, the internal impedance of the network across the load is to be determined as in previous theorem. Next open ckt voltage across load terminals is determined thus the amount of maximum power transfer becomes

$$P_{L,\max} = \frac{V_{oc}^2}{4R_L}$$

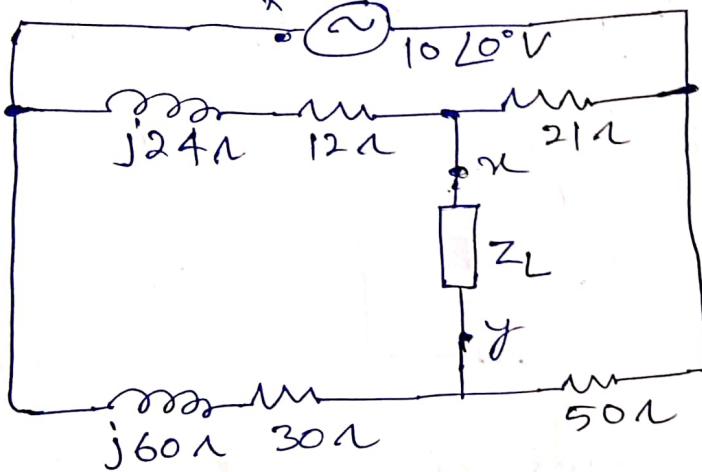Ex 12.44 :- On the network of fig below, find the value of Z_L , so that the transfer from source to load is max. Also find P_{max}



$V_{oc} = 10\angle 10^\circ$
 $= 6\angle 6^\circ$
 Similarly

Sol'n :- First remove the load Z_L , the internal impedance of ckt looking into terminals $x-y$ is

$$Z_{int} = Z_{x-y} = \frac{21(12+j24)}{21+12+j24} + \frac{50(30+j60)}{50+30+j60}$$

$$Z_{int} = (42.26 + j21.35)\Omega$$

for max power transfer

$$Z_L = Z_{int}^* = (42.26 - j21.35)\Omega$$

Next when source is present and load terminals open, let open ckt voltage is V_{oc} and potential of terminals x & y are V_x & V_y respectively

$$V_x = 10 \angle 0^\circ \cdot \frac{12 + j24}{12 + j24 + 2j} \\ = 6.577 \angle 27.43^\circ V$$


(A1)
[Voltage division rule]

Similarly, $V_y = 10 \angle 0^\circ \cdot \frac{30 + j60}{30 + j60 + 50} \\ = 6.71 \angle 26.56^\circ V$



$$\therefore V_{oc} = V_x - V_y \\ = 6.577 \angle 27.43^\circ - 6.71 \angle 26.56^\circ \\ = 0.1657 \angle 17^\circ V$$

$$\therefore P_{max} = \frac{V_{oc}^2}{4R_L} = \frac{0.1657}{4 \times 42.26} = 0.1624 \text{ mW}$$

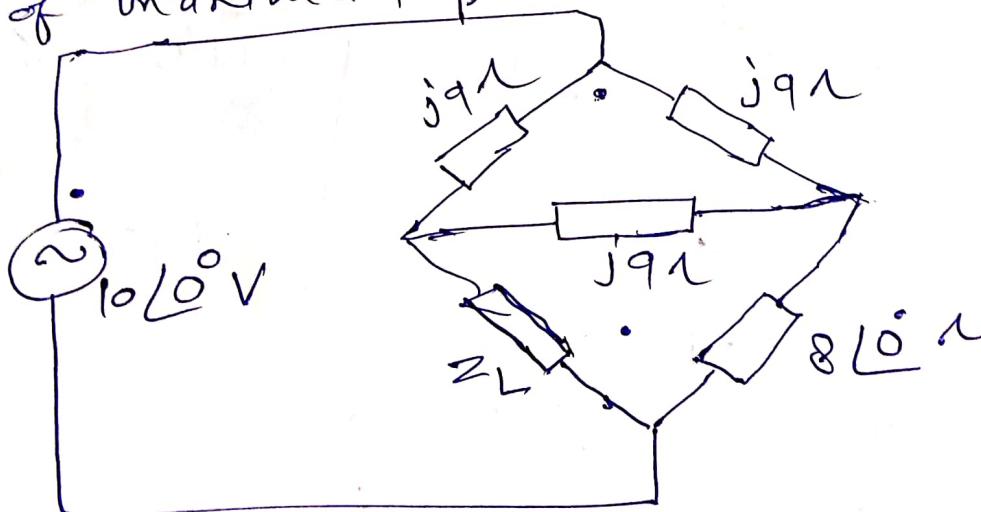Cx 12.45 :- Find the value of Z_L to have maximum power transfer from the $10 \angle 0^\circ$ voltage source. Also determine the amount of maximum power.





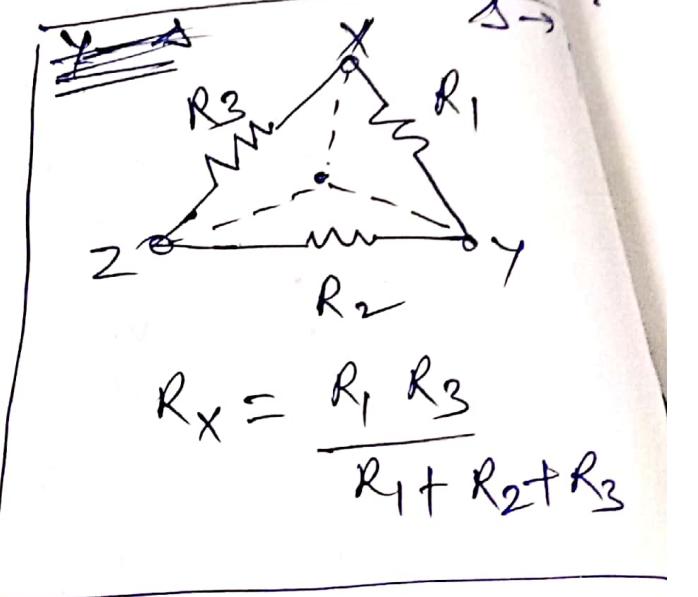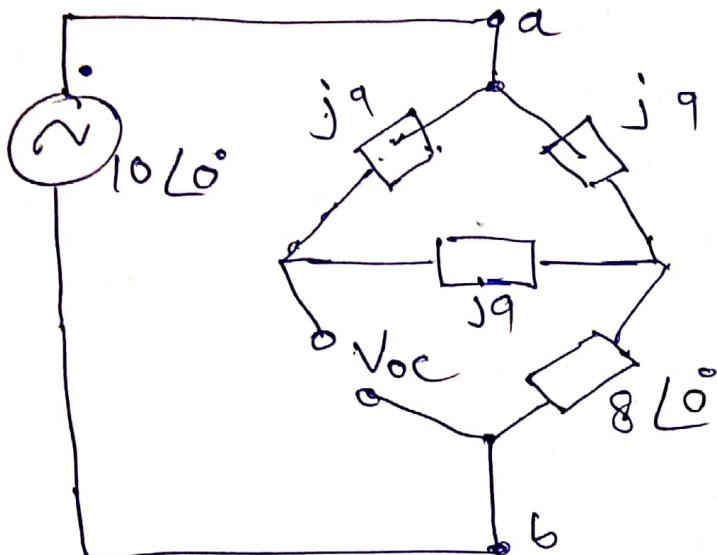Solⁿ :- Let us first remove load Z_L and find V_{oc}



convert $j9\Omega$ impedances for Δ to equivalent Y
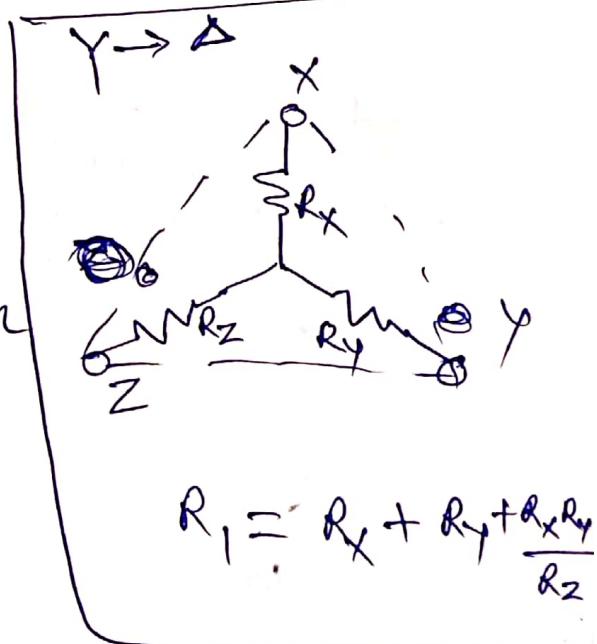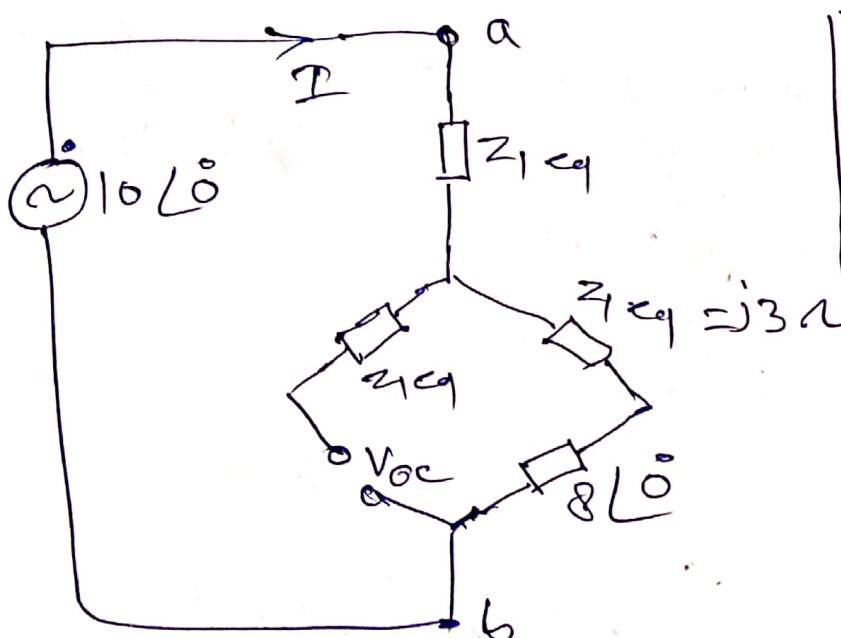
$$Z_{1eq} = \frac{j9 \cdot j9}{j9 + j9 + j9} = \frac{j9 \cdot j9}{3 \cdot j9} = j\frac{9}{3} = j3\Omega$$




$$I = \frac{10\angle0^\circ}{j3 + j3 + 8\angle0^\circ} = \frac{10\angle0^\circ}{8 + j6}$$

$$V_{OC} = I (Z_{eq} + j\omega L)$$


$$= \frac{10 \angle 0^\circ}{8+j6} (j3 + j0)$$

$$V_{OC} = 8.54 \angle -16.31^\circ V$$

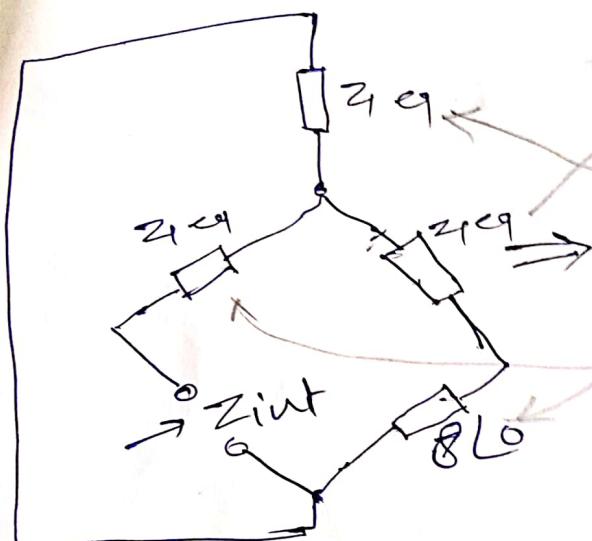To find out Z_{int} , open the load & replace voltage source by short circuit



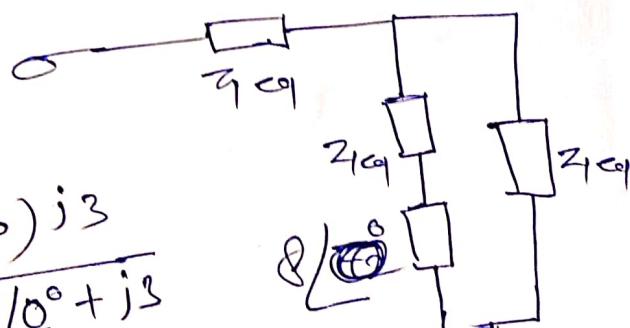Z_{eq} & $j\omega L$ in series are in parallel with Z_{eq} and this combn is parallel with Z_{eq}



$$\therefore Z_{int} = j3 + \frac{(j3 + 8\omega L)j3}{j3 + 8\omega L + j3}$$

$$= (0.72 + j5.46) \Omega$$

∴ for max power transfer

$$Z_L = \text{complex conjugate of } Z_{int}$$

$$= (0.72 - j5.46) \Omega$$

$$\text{Also } P_{Lmax} = \frac{V_{OC}^2}{4R_L} = \frac{(8.54)^2}{4 \times 0.72} = 25.32 W$$

A3

Reciprocity Theorem: - For a linear network containing generators and impedances, the ratio of voltage V introduced in one loop to the current I produced in any other loop is same as the ratio of voltage and current obtained if the position of voltage source V and the current source measured is interchanged.

To explain Reciprocity theorem consider ckt below:

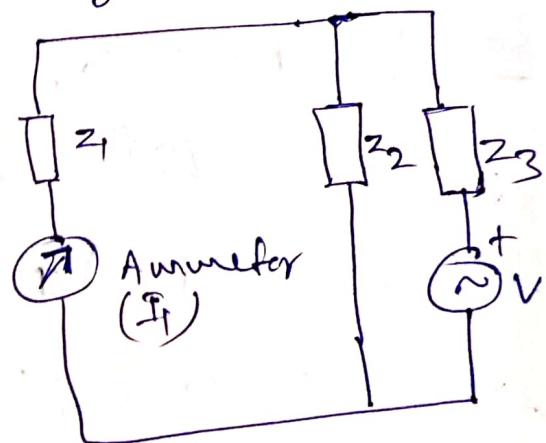
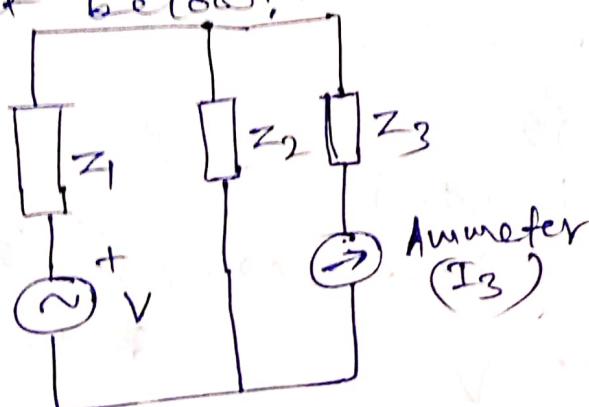


fig ④

Fig: Application of Reciprocity theorem

Let voltage V in fig ④ produces a current I_3 in the branch having impedance z_3 . In fig ⑤ we have just interchanged the position of voltage source and ammeter, as per reciprocity theorem

$$\boxed{\frac{V}{I_3} = \frac{V}{I_1}} \Rightarrow I_1 = I_3$$

Ex 12.10: - In fig (a) and fig (b) obtain V_o and establish reciprocity theorem.

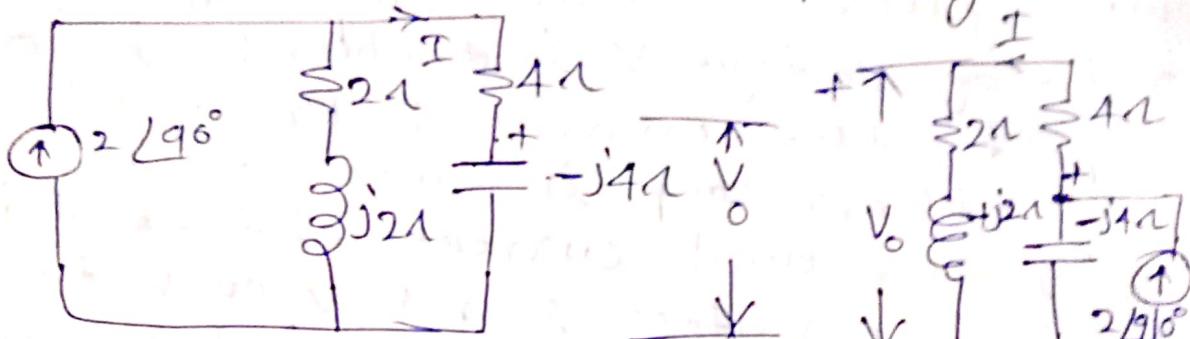


fig (a)

fig (b)

Soln: - from fig (a)

$$I = 2 \angle 90^\circ \times \frac{2+j2}{2+j2+4-j4}$$

$$\therefore V_o = (-j4) \neq = (-j4) \times 2 \angle 90^\circ \times \frac{(2+j2)}{(6-j2)}$$

$$= 3.58 \angle 63.43^\circ V$$

from fig (b)

$$V_o = I (2+j2) = 2 \angle 90^\circ \times \frac{-j4 \times (2+j2)}{-j4 + 4 + 2+j2}$$

$$= 3.58 \angle 63.43^\circ V$$

thus we see that in both the figures V_o is same with the interchange of sources, this proves the reciprocity theorem.

Tutorial / Assignment-2

Course: B.Tech

Section: EC-1,2,3& EI

Session: 2019-20

Sem: III

Subject: Network Analysis and Synthesis Sub. Code: KEC-303

- In the circuit of Fig.1, find the current through R_L connected across x-y terminals by utilising Thevenin's theorem. Verify the results by Norton's theorem also.

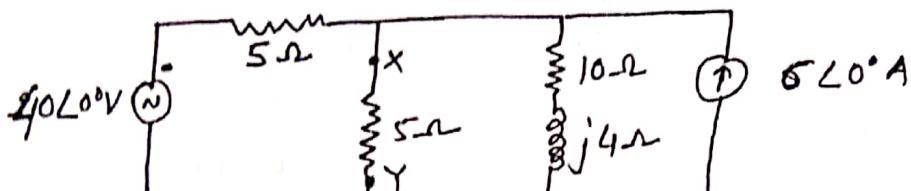


Fig. 1

- In the network of Fig.2, find the current through the 10 ohm resistance using Norton's theorem. Also find the power loss in the 10 ohm resistance.

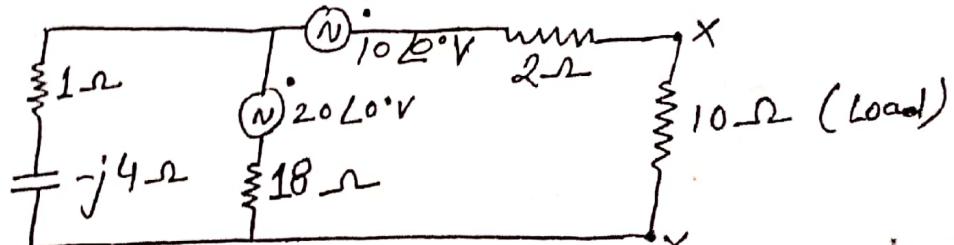


Fig. 2

- Find the Norton's equivalent circuit across x-y for the network shown in Fig.3.

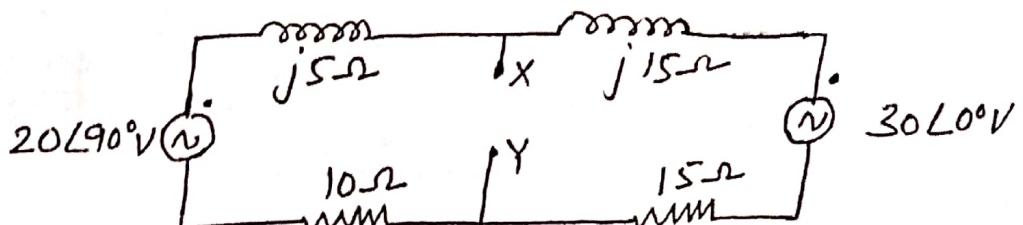


Fig. 3

- Find Thevenin's equivalent circuit across terminal a-b for the left part of the network of the circuit shown in the Fig.4



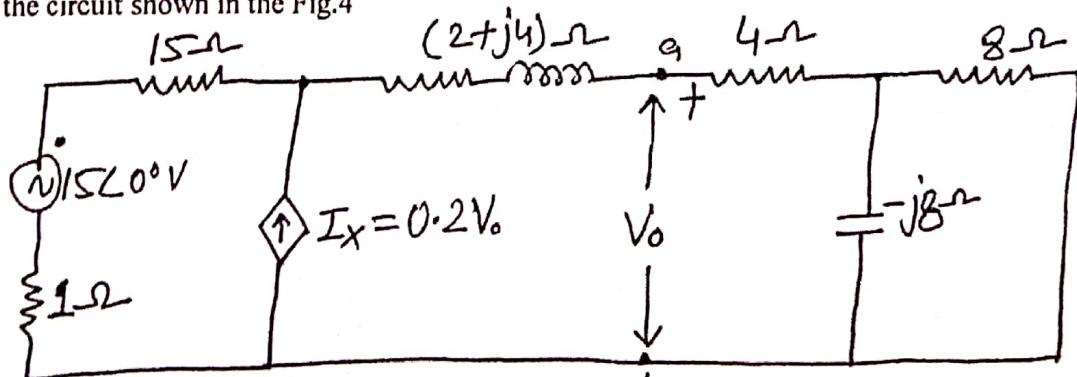


Fig. 4

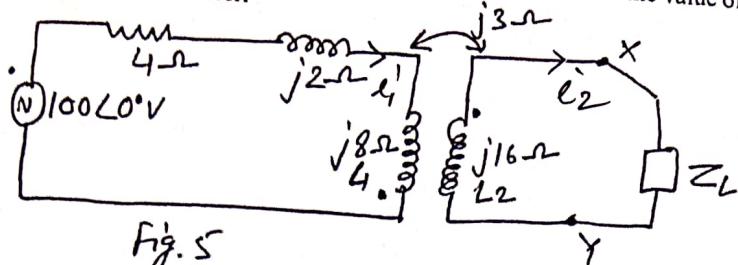5. Obtain equivalent circuit across x-y terminals in Fig.5 and find the value of Z_L to have maximum power transfer.



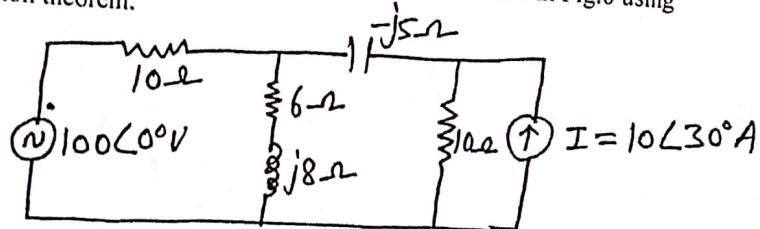6. Find the current through the capacitor of $(-j5)$ ohm reactance in Fig.6 using superposition theorem.



7. In the circuit shown in the Fig.7 determine the values of R and C so that the maximum power is absorbed by R. Determine the maximum power transferred to the load.



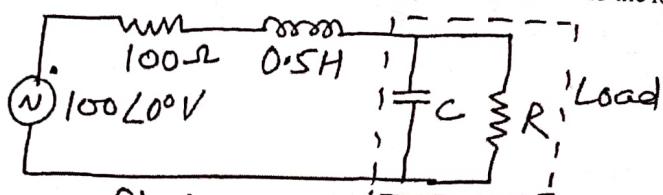


Fig. 7

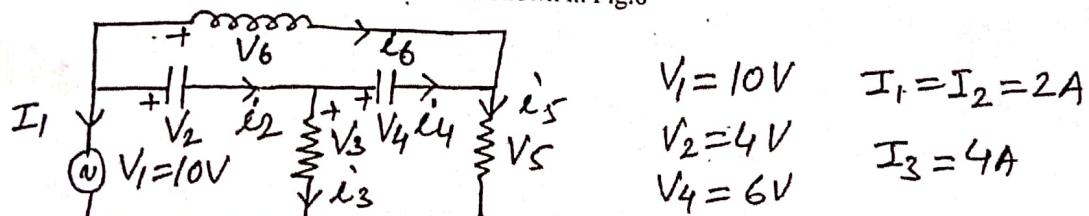8. Verify Tellegen's theorem in the network shown in Fig.8



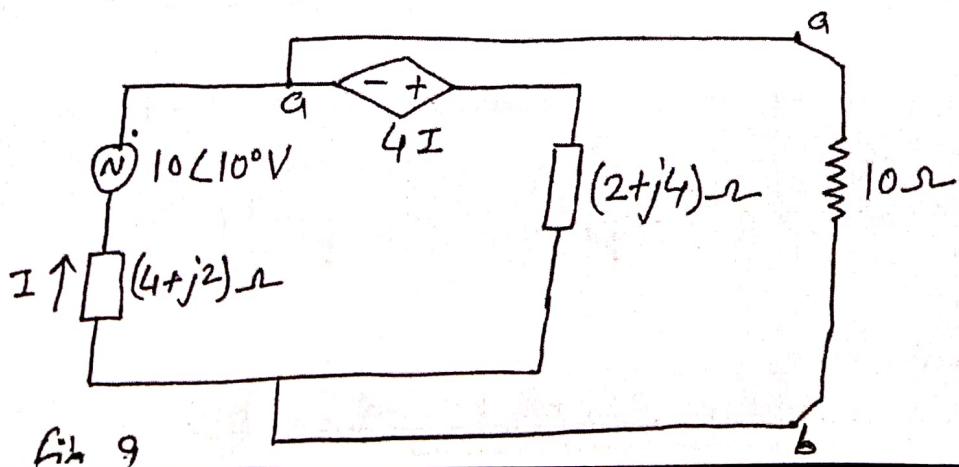9. Find Thevenin's equivalent circuit across a-b in the circuit of Fig.9 and find the current through 10 ohm resistance.



10. Using principle of superposition find the current in (-j4) ohm impedance in the circuit of Fig.10.

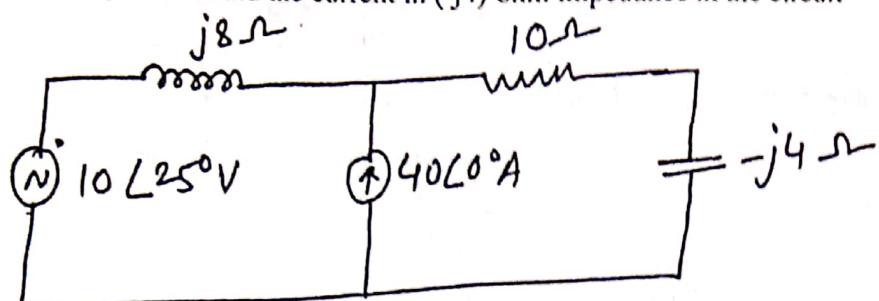


Fig. 10.

11. In the circuit shown in the Fig.11 two voltage sources act on the load impedance connected to terminal a-b. If the load impedance is variable, what load Z_L will draw the maximum power. Also calculate the maximum power.

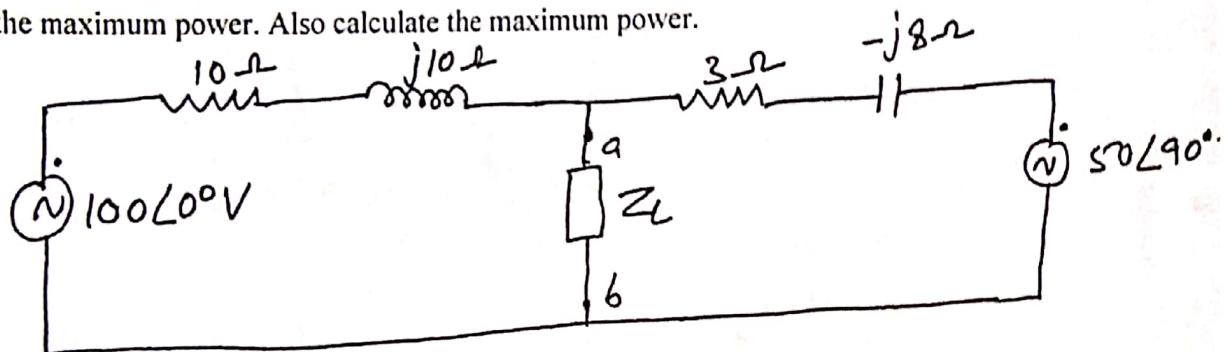


Fig. 11

12. Verify the Reciprocity theorem in the network shown in the Fig.12.

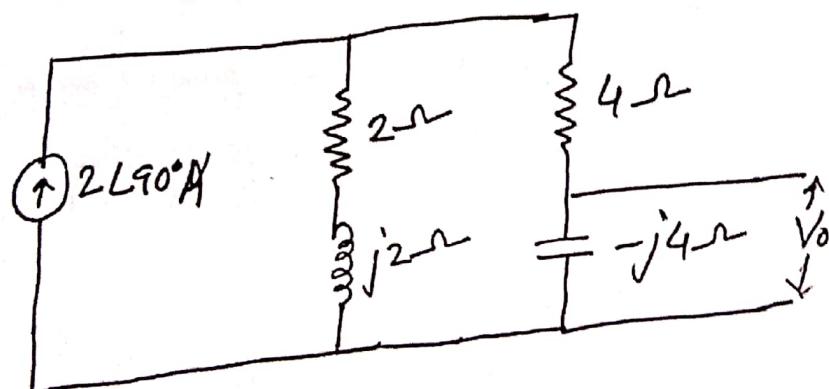


Fig. 12

13. State and Prove the maximum Power Transfer theorems.